

# Introduction to VHDL

Antoine Lavault<sup>12</sup>

<sup>1</sup>Apeira Technologies

<sup>2</sup>UMR CNRS 9912 STMS, IRCAM, Sorbonne Université

October 25, 2022



- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things

- VHDL = Very-High Speed Integrated Circuit High-Level Description Language. Not Verilog HDL.
- IEEE-approved standard for hardware description language
- High-level description language for both simulation and synthesis

Some terms we will use during the presentation :

- HDL - Hardware Description Language : a programming language used to describe a piece of hardware (duh)

To model a piece of hardware in HDL, two ways :

- Behavior modeling : A component is described by its input/output response
- Structural modeling : a component is described by interconnecting different components or primitives

- Register Transfer Level (RTL): a type of behavioural modeling for synthesis
- Synthesis : transposing the HDL description into an circuit, then optimizing the circuit.
- Process : a basic unit of execution in VHDL

- Only the functionality of the circuit is described, not the structure
- No specific hardware intent

## Example

Think of a bit left shifter.

Input :  $i_1, \dots, i_n$ , output :  $o_1, \dots, o_n$  If activated: for ii from n to 1: shift(i) := shift(i-1)  
output <=shift

- Describe the functionality and the structure of the circuit
- Call out the specific hardware



TODO

Two step process with feedback paths : synthesis and simulation.  
This is basically Test Driven Development

- Two types of constructs :
  - Simulation only
  - Synthesis and simulation
- VHDL language is (mostly) not case-sensitive
- A statement in VHDL ends with a ";" (semi-colon)
- VHDL is white-space insensitive (i.e indentation doesn't matter expect for the reader)
- Comments are added with "--" (two dashes)

- VHDL is a description language for complex digital circuits
- It is portable to any programmable digital platform
- High-level behavioural description from the specifications

- 1 VHDL Introduction
- 2 Programming in VHDL**
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things

 


Figure: And Gate

Way. Too. Hard.

The AND gate can be describe by what is "outside" and what is "inside":  
On the outside we have:

- two inputs :  $A$  and  $B$
- one output :  $Q$

On the inside, we have some magic powder, made of....  
Just kidding. It's a AND gate:  $Q = AB$

```
-- VHDL Code for AND gate
-- Header file declaration
library IEEE;
use IEEE.std_logic_1164.all;
-- Entity declaration
entity andGate is

    port(A : in STD_LOGIC;      -- AND gate input
          B : in STD_LOGIC;      -- AND gate input
          Q : out STD_LOGIC);    -- AND gate output
end andGate;
-- Architecture definition
architecture andLogic of andGate is
begin
    Q <= A AND B;
end andLogic;
```



- We have **libraries** in VHDL, and a library is made of **packages**.
- In the example above the library is IEEE and we use the package `std_logic_1164` (and especially, we import all of its content).
- To use the package, the keyword `use` is used, and `.all` shows we want to load all of the content of the library.
- Another useful library : STD\_NUMERIC

# Entity, or the outside

The syntax for the entity is shown below:

```
-- Entity declaration
entity entityName is
    port(list of ports);
end entityName;
```

A port is defined by a mode and a type. The 4 modes available are:

- in : for inputs
- out : for outputs
- inout : for bidirectional signals
- buffer : for outputs made to be fed back

As for the types, they are in general taken from the IEEE 1164 package:

- STD\_LOGIC for a scalar i.e a bit
- STD\_LOGIC\_VECTOR for a vector

- High-level portable description
  - Behavioral : data-flow, sequential process
  - Hierarchical : use of VHDL blocks and their connections
- Low-level hardware specific description
  - Uses proprietary of hardware-specific primitives
  - Can be used to force to use some part of the logic blocks on a FPGA.

The syntax for the entity is shown below:

```
-- Architecture declaration
architecture architectureName of entityName is
    -- internal signals and constants
    -- internal functions
begin
    -- dataflow description
    -- sequential description
end architectureName;
```

## Definition

A signal is an internal physical link between two elements.  
Inputs and outputs are external signals.

You should think of a signal as something you can look at with an oscilloscope.  
A signal can be instantiated between the keywords `Architecture` and `begin`:

```
signal signalName : signalType := initialValue;
```

## Remark

*All signals are strongly typed, like in C or Java!*

*This means conversion operations will happen often, between SIGNED and UNSIGNED especially.*

- bit: 0 or 1. Not really used in practice.
- boolean: True or False. Reference type for conditional structures
- STD\_LOGIC: 9 values:
  - 3 of them have a physical sense : 0,1 and Z
  - 6 others are used for simulation
    - U for uninitialized
    - X for unknown result
    - L for a signal that is probably 0
    - H for a signal that is probably 1
    - W for a signal non quantifiable by 0 or 1
    - - for "Do Not Care"

A vector can be thought of like an array of scalars.

- **STD\_LOGIC\_VECTOR**: is a vector of elements of type **STD\_LOGIC**

a: **STD\_LOGIC\_VECTOR**(3 **downto** 0);

b: **STD\_LOGIC\_VECTOR**(1 **to** 4);

- For VHDL vectors, the leftmost bit is the MSB. In this example,  $a(3)$  and  $b(1)$  are the MSB and  $a(0)$  and  $b(4)$  are the LSB.
- **SIGNED** and **UNSIGNED**: behave like **STD\_LOGIC\_VECTOR** but have arithmetic operations defined in **NUMERIC\_STD**. Conversion functions can be found in the **NUMERIC\_STD** package.

## ■ Mathematical types :

- INTEGER: 32 bit integer. Conversion functions exist to go from INTEGER to SIGNED or UNSIGNED. It can also be set to a certain range :

a: `integer range 0 to 20;` -- *an integer in [0,20]*

- NATURAL: integers greater or equal to 0.
- POSITIVE! integers greater or equal to 1
- REAL: float number, IEEE-754 standard.

## ■ Characters and Strings

- Very useful during simulation!!!
- CHAR: a character
- STRING: a string of characters.

## ■ Signals:

```
architecture Behavioural of syntaxExample is
    signal A: STD_LOGIC;
    signal B,C,D,E,F,G: STD_LOGIC;
    signal carry: STD_LOGIC := '1';
    signal HCounter: STD_LOGIC_VECTOR(9 downto 0);
    signal VCounter: STD_LOGIC_VECTOR(9 downto 0):=(others=>'0');
    signal op1, op2: STD_LOGIC_VECTOR(3 downto 0):="0000";
    signal seg7: STD_LOGIC_VECTOR(1 to 7);
    signal X,Y: INTEGER range 0 to 1023;
begin
    ...
```

## ■ Constants :

```
architecture Behavioural of syntaxExample is
    signal seg7: STD_LOGIC_VECTOR(1 to 7);
    constant number_1: STD_LOGIC_VECTOR(1to7):="0110000";
    constant number_2: STD_LOGIC_VECTOR(1to7):="1101101";
begin
    ...
```



- Assignment : `signal_name <= expression;`

If defined for the type in use, these operators also exist:

- Logic operators : and, or, not, nand, xor.
- Arithmetic operators (INTEGER, SIGNED, UNSIGNED): +, -, \*, /, mod (modulo), rem(remainder).
- Concatenation: for STD\_LOGIC, STD\_LOGIC\_VECTOR, CHAR and STRING.
- Comparison: <, >, <=, >=, =, /=

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL**
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things

## Example

We want to build a component that takes two inputs  $a$  and  $b$ , transform them through a AND gate that is attached to a D flip-flop with clock-enable and asynchronous reset.

We found two interesting components in a vendor-specific package :

- AND2 : two-inputs AND gate
- FDCE : D flip-flop with clock-enable and asynchronous reset

Let's import the package containing these components

```
library vendor;  
use vendor.specific.all;
```

We want to describe the outside of our component as such:

- *a* and *b* are inputs, *c* is an input
- A clock input with a clock enable pin
- An reset signal

A valid description in VHDL would be:

```
entity myComponent is
  port(a: in std_logic;
        b: in std_logic;
        c: out std_logic;
        clear: in std_logic;
        clk: in std_logic;
        clkEn: in std_logic);
end myComponent;
```

First, let's draw the circuit. If it hasn't been done before.

There is a clear place to put a signal : between the AND2 and the FDCE.

```
architecture behavioural of myComponent is  
    signal D_internal: std_logic;
```

To use the AND2 and FDCE components, we add the following to the architecture, before begin.

```
architecture behavioural of myComponent is
    signal D_internal: std_logic;
    component AND2
        port(i0: in std_logic;
            i1: in std_logic;
            o: out std_logic);
    end component;
    component FDCE
        port(...)
    end component;
```

# Using the library components, for real.

We only described the component to our architecture, to use them effectively, we write:

```
begin
  CMP1: AND2
    port map(i0=>a;
      i1=>b;
      o=>D_internal);
  CMP2: FDCE
    port map(
      C=>clk;
      CE=>clkEn;
      CLR=>clr;
      D=>D_internal;
      Q=>c);
end behavioural;
```

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling**
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things



Between `begin` and `end`, lies the concurrent domain.

This means operations written in this domain are executed in parallel when possible.

There are three main components in the concurrent domain :

- Dataflow elements
  - Simple assignments
  - Conditional assignments : `when ... else ...`
  - Selected signal assignments : `with ... select ...`
- Sequential processes

## An example - AND gate

This is how you write a when ... else ...:

```
output <= '1' when in1='1' = 1 and in2='1'  
      else '0' when in1='1' = 1 and in2='0'  
      else '0' when in1='0' = 1 and in2='1'  
      else '0' when in1='0' = 1 and in2='0'  
      else '0';
```

Why else 0; at the end? Keep in mind that STD\_LOGIC elements have 9 values!

## An example - AND gate

The following is also valid:

```
output <= '1' when in1='1' = 1 and in2='1' else '0';
```

and this one as well:

```
signal inputs: STD_LOGIC_VECTOR(1 to 2);  
begin  
    inputs <= in1 & in2;  
    output <= '1' when inputs = "11" else '0';  
end architecture;
```

## Going further-ALU

Let's design an ALU of with 8bits inputs/output and two operations ADD and SUBSTRACT.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL
use IEEE.NUMERIC_STD;
entity alu is
    port(ina: std_logic_vector(7 downto 0);
         inb: std_logic_vector(7 downto 0);
         operation: std_logic;
         output: std_logic_vector(7 downto 0));
end alu;
architecture behavioural of alu is
begin
    output <= STD_LOGIC_VECTOR(SIGNED(ina) + SIGNED(inb))
        when operation = '0'
    else STD_LOGIC_VECTOR(SIGNED(ina) - SIGNED(inb))
        when operation = '1'
    else "00000000";
end behavioural;
```

# Selective assignement

Back to the AND gate example...

```
signal inputs: STD_LOGIC_VECTOR(1 to 2);  
begin  
    inputs <= in1 & in2;  
    output <= '1' when inputs = "11" else '0';  
end architecture;
```

can be transformed in:

```
signal inputs: STD_LOGIC_VECTOR(1 to 2);  
begin  
    with inputs select  
        sortie <= '1' when '11',  
                 '0' when others;  
end architecture;
```

## Warning

Always put when others to handle cases not described.

## With/select statement-ALU

The ALU example with the "with/select" statement would be:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD;
entity alu is
    port(ina: std_logic_vector(7 downto 0);
          inb: std_logic_vector(7 downto 0);
          operation: std_logic;
          output: std_logic_vector(7 downto 0));
end alu;
architecture behavioural of alu is
begin
    with operation select
        output<=STD_LOGIC_VECTOR(SIGNED(ina) + SIGNED(inb))
            when operation = '0'
            STD_LOGIC_VECTOR(SIGNED(ina) - SIGNED(inb))
            when operation = '1'
            (others=>0) when others; -- returns an adequately sized
end behavioural;
```

# Testing ?

Well, we better have a way to test these snippets of code...  
Later. Too late to write a lecture.

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes**
- 6 Test-benches
- 7 Miscalenous things



We have seen not so long ago that the concurrent domain allows the execution of sequential processes.

In this domain, we will be able to :

- use C-like structures
- describe combinational logic blocks in a different way
- easily handle synchronous phenomenon i.e clock ticks.
- test-benches

How to do that? Describe a process:

```
processName : process(sensitivity_list)
```

- Sensitivity list: list of signals whose change of state launch the process
- No sensitivity ? Remove the parenthesis, executed unconditionally.
- Naming the process is not necessary.

```
processName : process(sensitivity_list)
    -- declare internal variables
    -- declare constants
begin
    -- sequential process <-> line order matters
end processName;
```

- The syntax is awfully similar...
- But they have totally different meanings:
  - A signal physically exists in the component (unless some optimisation are applied at synthesis time)
  - A variable only exists in the process (limited scope) and is just a helper when writing the equations in the process
- And different assignation behaviours:
  - In a process, a signal is assigned with  $\leq$  and the assignation will be effective only when the process is exited !
  - In a process, a variable is assigned with  $:=$  and it's instantaneous.

- Simple assignments : `<=` for signals, `:=` for variables
- Conditional/selective assignments : ok in VHDL-2008. In general, not the default version of VHDL.
- Conditional structures `if.then.elsif.else.endif`;

```
case var is
  when val => action1; -- action if var = val
  when vald to valf => action2; -- if var is between vald and valf
  when val1|val2|valn => action3; -- if var is val1, val2 or valn
  when others => action4; -- deal with the rest
end case;
```

For loop:

```
for index in start_value to end_value loop
  -- index etc... are integers or subtype of integers
  -- actions to do in the loop
  -- etc...
end loop;
```

While loop:

```
while condition loop
  -- actions to do in the loop
end loop;
```

Ensure the condition becomes false at some point...

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches**
- 7 Miscalenous things

Let's take the AND gate we have seen some pages ago.  
We can test it by:

- Playing with a simulator
- Writing tests in VHDL → exhaustive and with much more controls.



A test-bench can be described as a VHDL component with:

- No inputs or outputs (a sealed box)
- Internal signals to test the unit under test
- a declaration of the unit under test
- After `begin`, instantiate the unit under test
- Test signals (generated within the test-bench)

Let's write this !

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL
-- No inputs or outputs
entity andGate_tb is
end andGate_tb;
architecture behavioural of andGate_tb is
    -- internal signals, used as stimuli
    signal A,B,Q: STD_LOGIC;
    -- uut declaration
    component andGate is
    port(A : in STD_LOGIC;
         B : in STD_LOGIC;
         Q : out STD_LOGIC);
    end component;
begin
---
```

## Let's write this ! Cont.

```
begin
  --- instantiate the unit under test
  uut: andGate port map(
    A=>A,
    B=>B,
    Q=>Q);
  A_stimuli: process
  begin
    A <= '0'; wait for 5ns;
    A <= '1'; wait for 5ns;
  end process A_stimuli;
  B_stimuli: process
  begin
    B <= '0'; wait for 10ns;
    B <= '1';
  end process B_stimuli;
end behavioural;
```

- 1 VHDL Introduction
- 2 Programming in VHDL
- 3 Structural VHDL
- 4 Dataflow modeling
- 5 Sequential processes
- 6 Test-benches
- 7 Miscalenous things**

- A `STD_LOGIC_VECTOR` is a vector of `STD_LOGIC`. And that's it. Is it an integer, a float, a banana? Can I add it, can I multiply it, can I peel it?
- This is why we use `SIGNED` and `UNSIGNED`. The underlying data is still `STD_LOGIC` but we now know how to handle it.
- Conversion function: `TO_SIGNED`, `TO_UNSIGNED`, `TO_INTEGER` (in `NUMERIC_STD`)
- Operations : they are defined in `NUMERIC_STD` !

- An attribute in VHDL is a meta property that's attached to a type or object.
- It's useful to know a signal behaves → clock edges
- Some are used in simulation only e.g `last_event`

We also define what is a transaction:

- A signal is assigned a value
- The assignment does not necessarily change the value.

- Bound to the signal declaration:
  - TODO
- Bound to the signal evolution
  - event if the signal got its value changed when entering a process
  - event if the signal got a transaction during the current process
  - last\_event(simulation only) elapsed time since last event
  - last\_value value before the last event
  - last\_active(simulation only) elapsed time since last transaction

Usage: find a rising edge on the clock signal:

```
clk'event' and clk'last_value'=0 and clk=1
```

There are also the functions `rising_edge` and `falling_edge` from the 1164 package:

```
rising_edge(clk)  
falling_edge(clk)
```





