



MSCV/ESIREM

Real-Time Imaging and Control Practice

Antoine Lavault
antoine.lavault@u-bourgogne.fr

「 VHDL 1 」

Most of the exercises will require you to write VHDL on paper. Pay attention to the syntax.

└ Problem 1 ▸

Create a D flip-flop with :

1. 2 inputs : D, clk
2. 1 output : q

└ Problem 2 ▸

Create an synchronous 8-bit counter with asynchronous reset :

1. 2 inputs : reset, clk
2. 1 output : s

└ Problem 3 ▸

Create a NOR gate with a generic number of inputs, greater or equal to 4.
You can use the following entity:

```
entity NORgate is
    generic (
        W : positive := 4 -- number of inputs of the NOR gate
    );
    port (
        input : in std_logic_vector(W - 1 downto 0);
        output : out std_logic
    );
end NORgate;
```

Problem 4

Create an 8-bit shift register :

NB: In digital circuits, a shift register is a cascade of D flip flops, sharing the same clock, in which the output of each flip-flop is connected to the 'data' input of the next flip-flop in the chain, resulting in a circuit that shifts by one position the 'bit array' stored in it, 'shifting in' the data present at its input and 'shifting out' the last bit in the array, at each transition of the clock input.

Problem 5

Create a multiplexer (mux) with :

1. 2 inputs : data(8),sel(3)
2. 1 output : s(1)
3. 1 CLK for synchronous behaviour

Problem 6

Create a VHDL Design that allow the same behavior of the common-cathoded BCD¹-decoder (figure : 2), the 74LS48 IC².

A BCD-decoder is used to display value on 7-segment display (see figure : 1).

 


Figure 1: Example of 7 segments display

NB : 7-segment LED (Light Emitting Diode) or LCD (Liquid Crystal Display) type displays, provide a very convenient way of displaying information or digital data in the form of numbers, letters or even alpha-numerical characters.

Typically 7-segment displays consist of seven individual coloured LED's (called the segments), within one single display package. In order to produce the required numbers or HEX characters from 0 to 9 and A to F respectively, on the display the correct combination of LED segments need to be illuminated and BCD to 7-segment Display Decoders.

A standard 7-segment LED display generally has 8 input connections, one for each LED segment and

¹Binary-Coded Decimal

²<http://pdf.datasheetcatalog.com/datasheet/motorola/74LS48.pdf>

 


Figure 2: BCD-decoder

one that acts as a common terminal or connection for all the internal display segments. Some single displays have also have an additional input pin to display a decimal point in their lower right or left hand corner.

Problem 7

Propose a VHDL component with a N -bit input x ($N \geq 8$) with an output at logic level high when there is at least 4 '1' and 4 '0' in x .

Problem 8

The following code describe a finite state-machine. What ki

```
-- A Mealy machine has outputs that depend on both the state and
-- the inputs.          When the inputs change, the outputs are updated
-- immediately, without waiting for a clock edge. The outputs
-- can be written more than once per state or per clock cycle.
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mealy_4s IS
    PORT (
        clk : IN STD_LOGIC;
        data_in : IN STD_LOGIC;
        reset : IN STD_LOGIC;
        data_out : OUT STD_LOGIC_VECTOR(1 DOWNT0 0)
    );
END ENTITY;

ARCHITECTURE rtl OF mealy_4s IS
    -- Build an enumerated type for the state machine
    TYPE state_type IS (s0, s1, s2, s3);
    -- Register to hold the current state
    SIGNAL state : state_type;
BEGIN
```

```

PROCESS (clk, reset)
BEGIN
    IF reset = '1' THEN
        state <= s0;
    ELSIF (rising_edge(clk)) THEN
        -- Determine the next state synchronously, based on
        -- the current state and the input
        CASE state IS
            WHEN s0 =>
                IF data_in = '1' THEN
                    state <= s1;
                ELSE
                    state <= s0;
                END IF;
            WHEN s1 =>
                IF data_in = '1' THEN
                    state <= s2;
                ELSE
                    state <= s1;
                END IF;
            WHEN s2 =>
                IF data_in = '1' THEN
                    state <= s3;
                ELSE
                    state <= s2;
                END IF;
            WHEN s3 =>
                IF data_in = '1' THEN
                    state <= s3;
                ELSE
                    state <= s1;
                END IF;
        END CASE;
    END IF;
END PROCESS;

-- Determine the output based only on the current state
-- and the input (do not wait for a clock edge).
PROCESS (state, data_in)
BEGIN
    CASE state IS
        WHEN s0 =>
            IF data_in = '1' THEN
                data_out <= "00";
            ELSE
                data_out <= "01";
            END IF;
        WHEN s1 =>

```

```

        IF data_in = '1' THEN
            data_out <= "01";
        ELSE
            data_out <= "11";
        END IF;
    WHEN s2 =>
        IF data_in = '1' THEN
            data_out <= "10";
        ELSE
            data_out <= "10";
        END IF;
    WHEN s3 =>
        IF data_in = '1' THEN
            data_out <= "11";
        ELSE
            data_out <= "10";
        END IF;
    END CASE;
END PROCESS;

END rtl;

```

What is the function described by this finite state-machine?

Problem 9

Create the state-machine represented of the following pictures (figure : 3) :

You can assume the output is the number of the state (i.e $S0 \rightarrow 0$, $S1 \rightarrow 1$ etc...)

Hint: you can use custom sub-types to encode the states like

```

type state_type is (idle, statel, state2,...);
signal present_state, next_state: state_type;

```

Problem 10


The parity function is true if the number of bits equal to '1' at its input is even.

For instance, this function is true for 0000; 1111; 1001 and false for 0001; 0111.

```

entity parity is
    generic (
        W : positive := 4); -- number of input bits
    port (
        I : in std_logic_vector(W - 1 downto 0);
        F : out std_logic -- 1 if parity, 0 if not.
    );
end parity;

```

 

State Transition Diagram

Figure 3: State machine

Write a testbench completely checking the `parity` module with a arbitrary number of bits.

Remark 1. You can instantiate an UUT with the following snippet:

```
UUT: entity f (arch) generic map (W) port map (testVector, response);
```

You can use VHDL functions or external files to get the expected test responses.

You can also use the `assert...report` statement.

Finally, it is easy to iterate over N bits with a `for` loop and get all the values possible.

Problem 11

A billionaire called Bruce W. fears for the privacy of its "special" affairs and want to add a CCTV system to his manor.

The cameras used in the system are numbered $0, 1, 2, 3 \dots N$ and can detect intruders whatever the time of day is. When an intruder is detected, the camera sends a signal on a dedicated data path.

To connect all these cameras, you are tasked to design a system that activates an alarm when at least one camera detects an intruder and give the ID number of the activated camera (as a binary number). Since

Mr W. is feared by his enemies, and for good reasons, it's not expected to see more than one intruder at a time. But the system should raise an error flag if by any chance more than one camera detected an intruder.

1. Give a VHDL code describing the case with 4 cameras
2. Same question with a generic number of cameras.